PRASHANT KANWAL

Nand2Tetris | Lab 1 Report

Roll No:	2501730468	**Course:**	B.Tech CSE AIML
Subject:	Nand2Tetris	**Section:**	G

Contents

Each chip below includes its HDL code and the Hardware Simulator output.

01	And.hdl	Project 1	11	Or8Way.hdl	Project 1
02	Not.hdl	Project 1	12	Mux4Way16.hdl	Project 1
03	Or.hdl	Project 1	13	Mux8Way16.hdl	Project 1
04	Xor.hdl	Project 1	14	DMux4Way.hdl	Project 1
05	Mux.hdl	Project 1	15	DMux8Way.hdl	Project 1
06	DMux.hdl	Project 1	16	HalfAdder.hdl	Project 2
07	Not16.hdl	Project 1	17	FullAdder.hdl	Project 2
08	And16.hdl	Project 1	18	Add16.hdl	Project 2
09	Or16.hdl	Project 1	19	Inc16.hdl	Project 2
10	Mux16.hdl	Project 1	20	ALU.hdl	Project 2

01 And.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/And.hdl
/**
 * And gate:
 * if (a and b) out = 1, else out = 0
 */
CHIP And {
    IN a, b;
    OUT out;

    PARTS:
    Nand(a=a, b=b, out=nand1);
    Nand(a=nand1, b=nand1 ,out=out);
}
```

Screenshot (Hardware Simulator output):

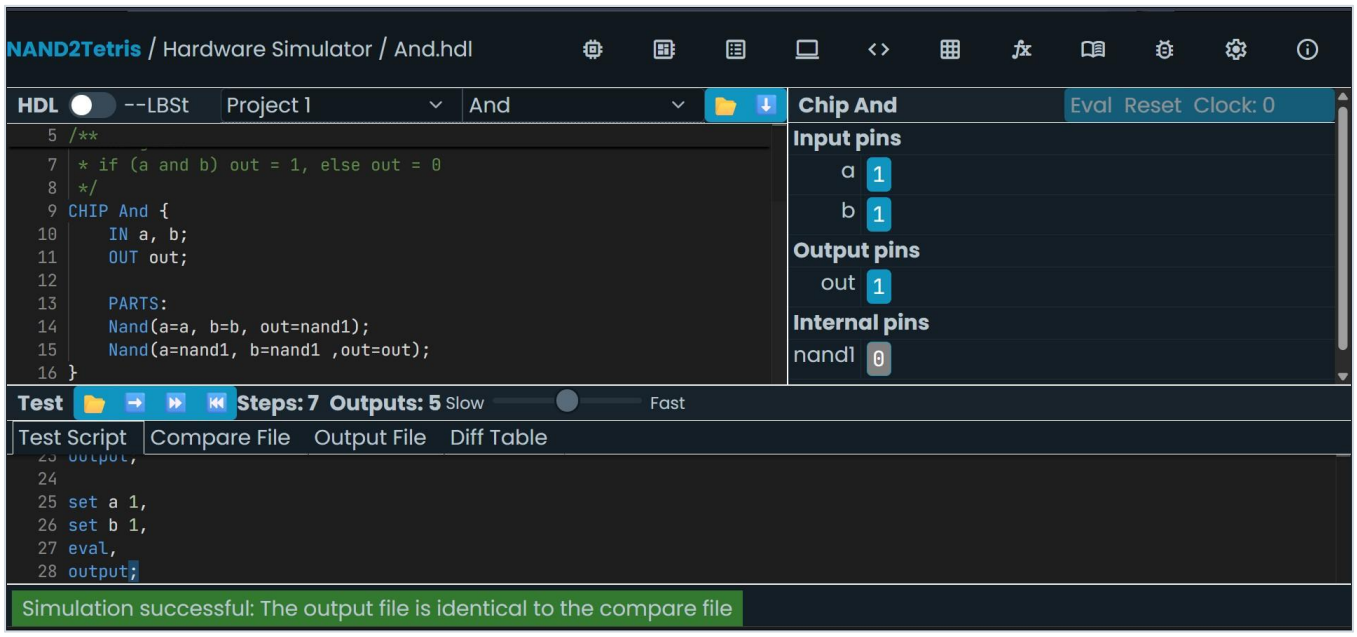

02 Not.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Not.hdl
/**
 * Not gate:
 * if (in) out = 0, else out = 1
 */
CHIP Not {
    IN in;
    OUT out;

    PARTS:
    Nand(a=in,b=in,out=out);
}
```

Screenshot (Hardware Simulator output):

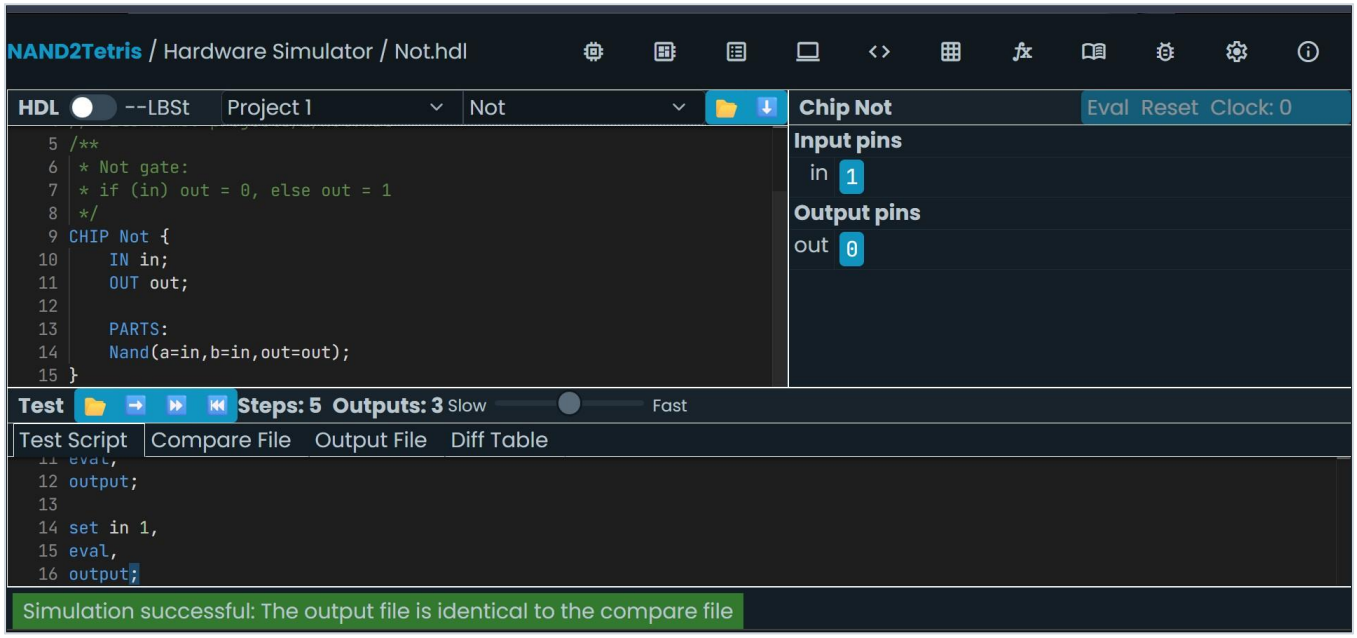

03 Or.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Or.hdl
/**
 * Or gate:
 * if (a or b) out = 1, else out = 0
 */
CHIP Or {
    IN a, b;
    OUT out;

    PARTS:
    Nand(a=a, b=a,out=nand1);
    Nand(a=b, b=b, out=nand2);
    Nand(a=nand1 , b=nand2 , out=out );
}
```

Screenshot (Hardware Simulator output):

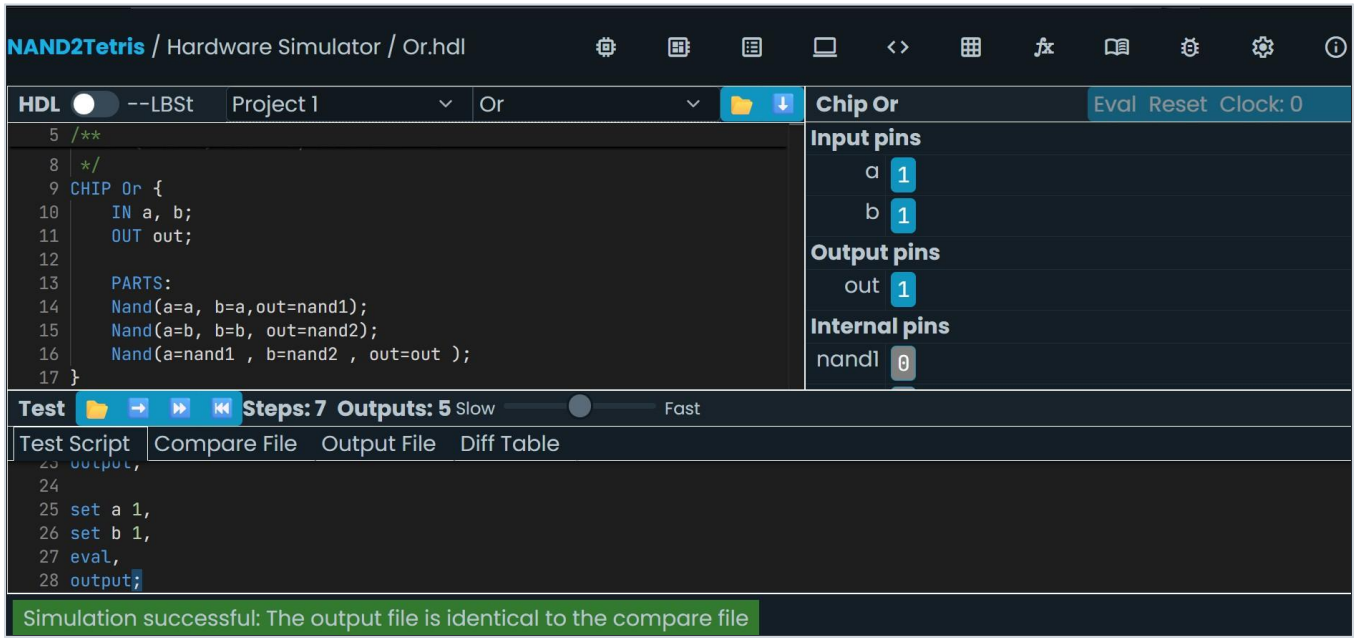

04 Xor.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Xor.hdl
/**
 * Exclusive-or gate:
 * if ((a and Not(b)) or (Not(a) and b)) out = 1, else out = 0
 */
CHIP Xor {
    IN a, b;
    OUT out;

    PARTS:
    Nand(a=a , b=b , out=c );
    Nand(a=a , b=c , out=d );
    Nand(a=c , b=b , out=e );
    Nand(a=d , b=e , out=out );
}
```

Screenshot (Hardware Simulator output):

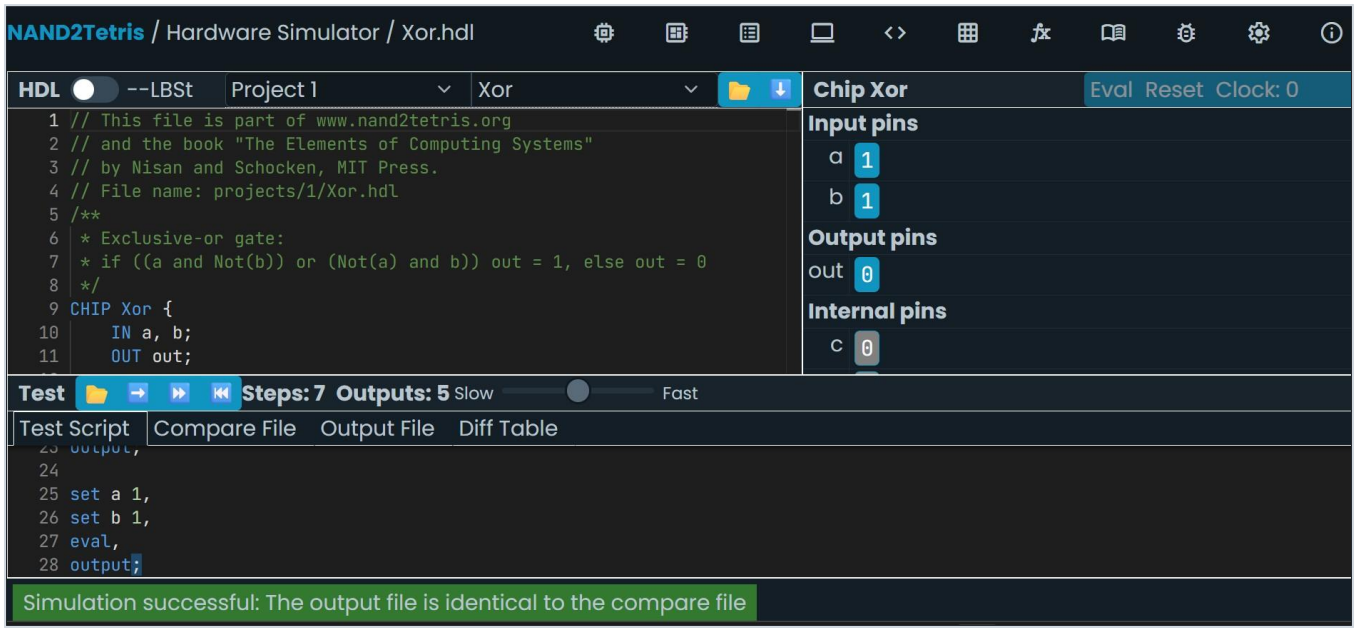

05 Mux.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Mux.hdl
/**
 * Multiplexor:
 * if (sel = 0) out = a, else out = b
 */
CHIP Mux {
    IN a, b, sel;
    OUT out;

    PARTS:
    Not(in=sel, out=asel);
    And(a=a, b=asel, out=a1);
    And(a=b, b=sel, out=b1);
    Or(a=a1, b=b1, out=out);
}
```

Screenshot (Hardware Simulator output):

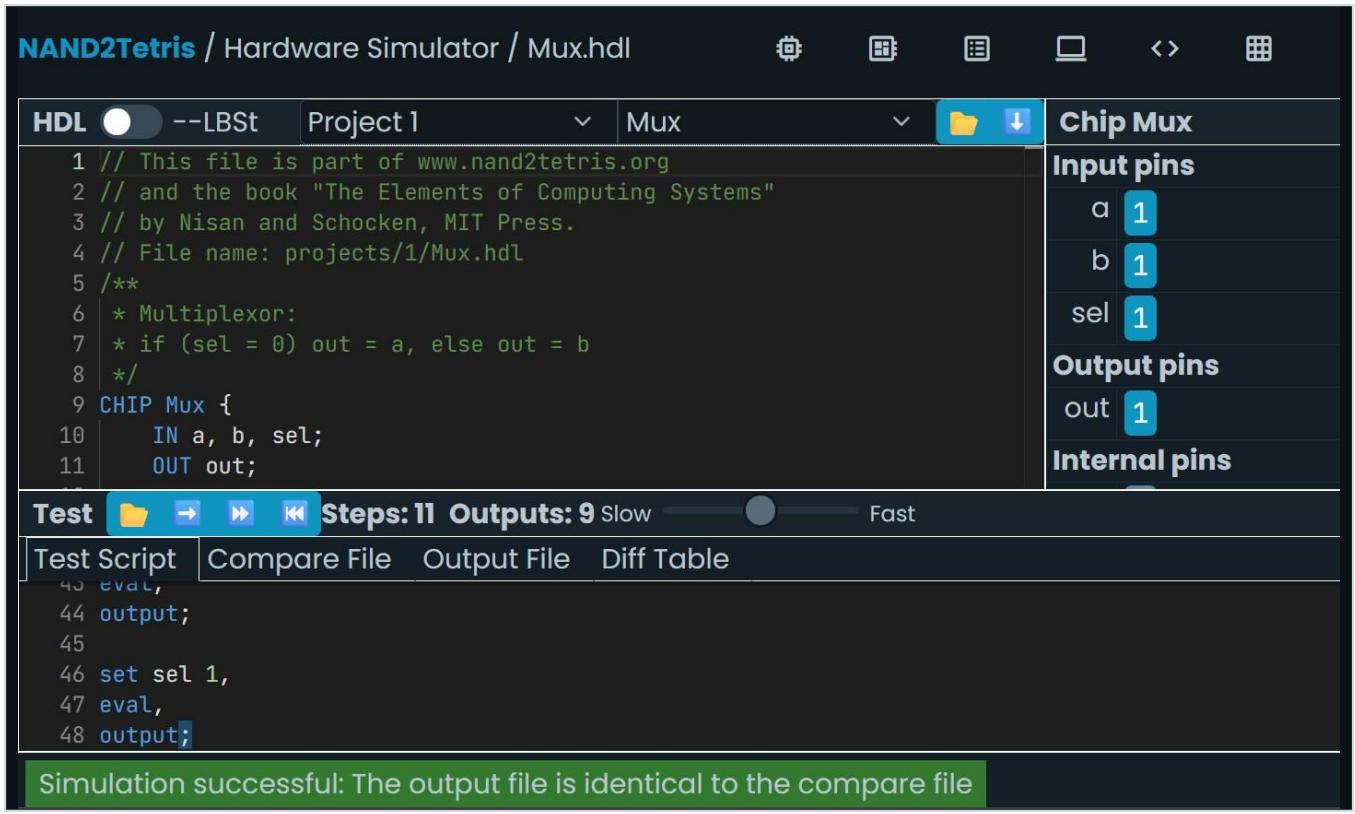

06 DMux.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/DMux.hdl
/**
 * Demultiplexor:
 * [a, b] = [in, 0] if sel = 0
 *          [0, in] if sel = 1
 */
CHIP DMux {
    IN in, sel;
    OUT a, b;

    PARTS:
    Not(in=sel, out=nsel);
    And(a=in, b=nsel, out=a);
    And(a=in, b=sel, out=b);
}
```

Screenshot (Hardware Simulator output):

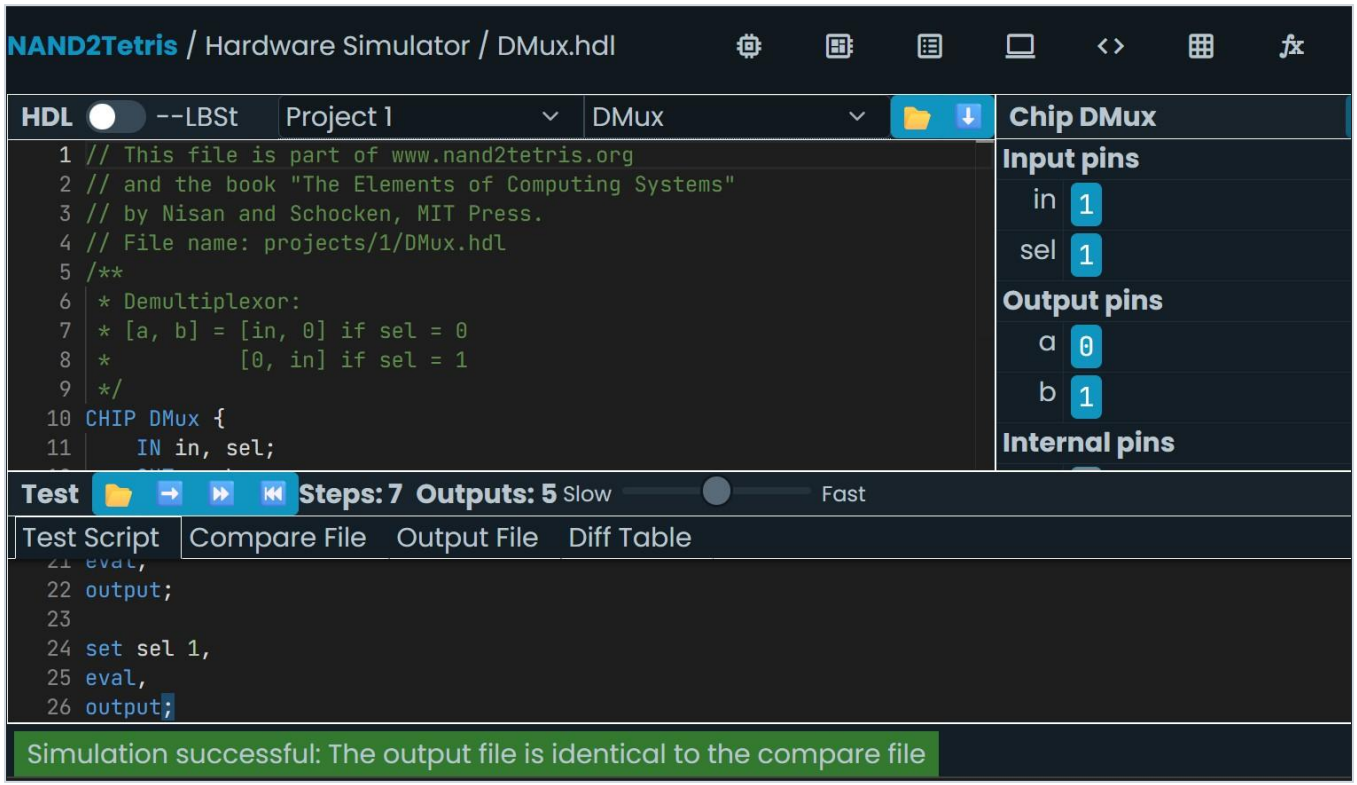

07 Not16.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/01/Not16.hdl
/**
 * 16-bit Not gate:
 * for i = 0, ..., 15:
 * out[i] = Not(a[i])
 */
CHIP Not16 {
    IN in[16];
    OUT out[16];

    PARTS:
    Not(in=in[0], out=out[0]);
    Not(in=in[1], out=out[1]);
    Not(in=in[2], out=out[2]);
    Not(in=in[3], out=out[3]);
    Not(in=in[4], out=out[4]);
    Not(in=in[5], out=out[5]);
    Not(in=in[6], out=out[6]);
    Not(in=in[7], out=out[7]);
    Not(in=in[8], out=out[8]);
    Not(in=in[9], out=out[9]);
    Not(in=in[10], out=out[10]);
    Not(in=in[11], out=out[11]);
    Not(in=in[12], out=out[12]);
    Not(in=in[13], out=out[13]);
    Not(in=in[14], out=out[14]);
    Not(in=in[15], out=out[15]);
}
```

Screenshot (Hardware Simulator output):

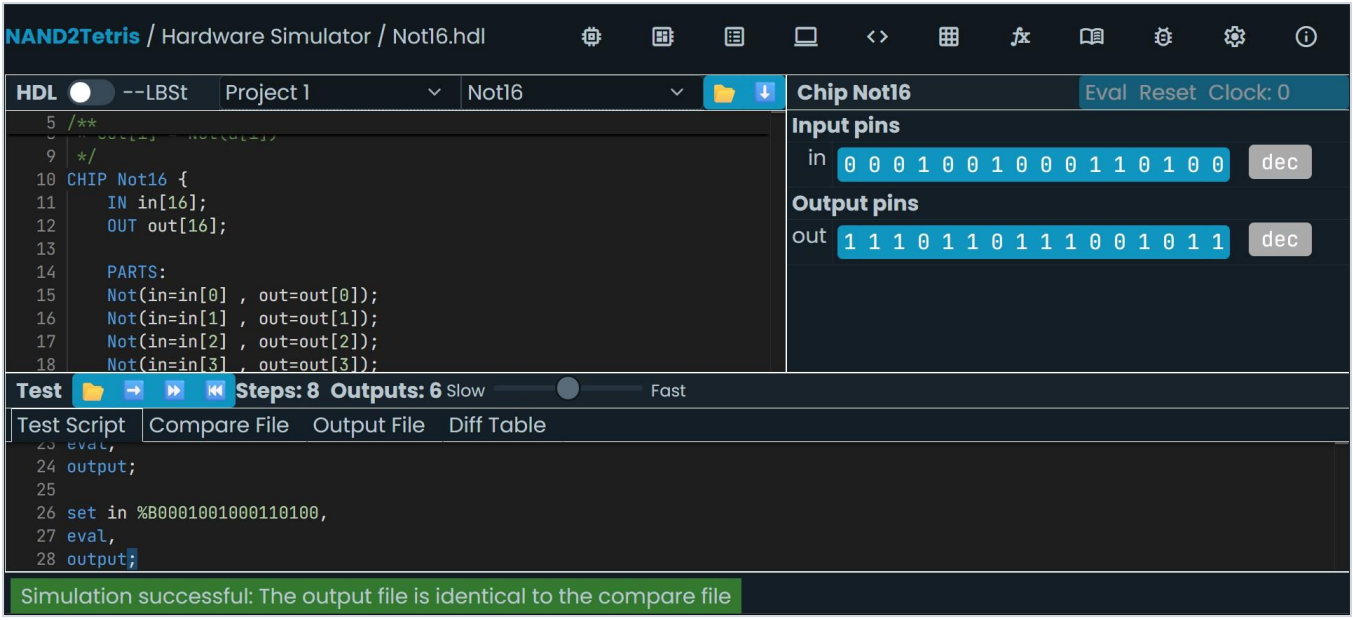

08 And16.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/And16.hdl
/**
 * 16-bit And gate:
 * for i = 0, ..., 15:
 * out[i] = a[i] And b[i]
 */
CHIP And16 {
    IN a[16], b[16];
    OUT out[16];

    PARTS:
    And(a=a[0], b=b[0], out=out[0]);
    And(a=a[1], b=b[1], out=out[1]);
    And(a=a[2], b=b[2], out=out[2]);
    And(a=a[3], b=b[3], out=out[3]);
    And(a=a[4], b=b[4], out=out[4]);
    And(a=a[5], b=b[5], out=out[5]);
    And(a=a[6], b=b[6], out=out[6]);
    And(a=a[7], b=b[7], out=out[7]);
    And(a=a[8], b=b[8], out=out[8]);
    And(a=a[9], b=b[9], out=out[9]);
    And(a=a[10], b=b[10], out=out[10]);
    And(a=a[11], b=b[11], out=out[11]);
    And(a=a[12], b=b[12], out=out[12]);
    And(a=a[13], b=b[13], out=out[13]);
    And(a=a[14], b=b[14], out=out[14]);
    And(a=a[15], b=b[15], out=out[15]);
}
```

Screenshot (Hardware Simulator output):

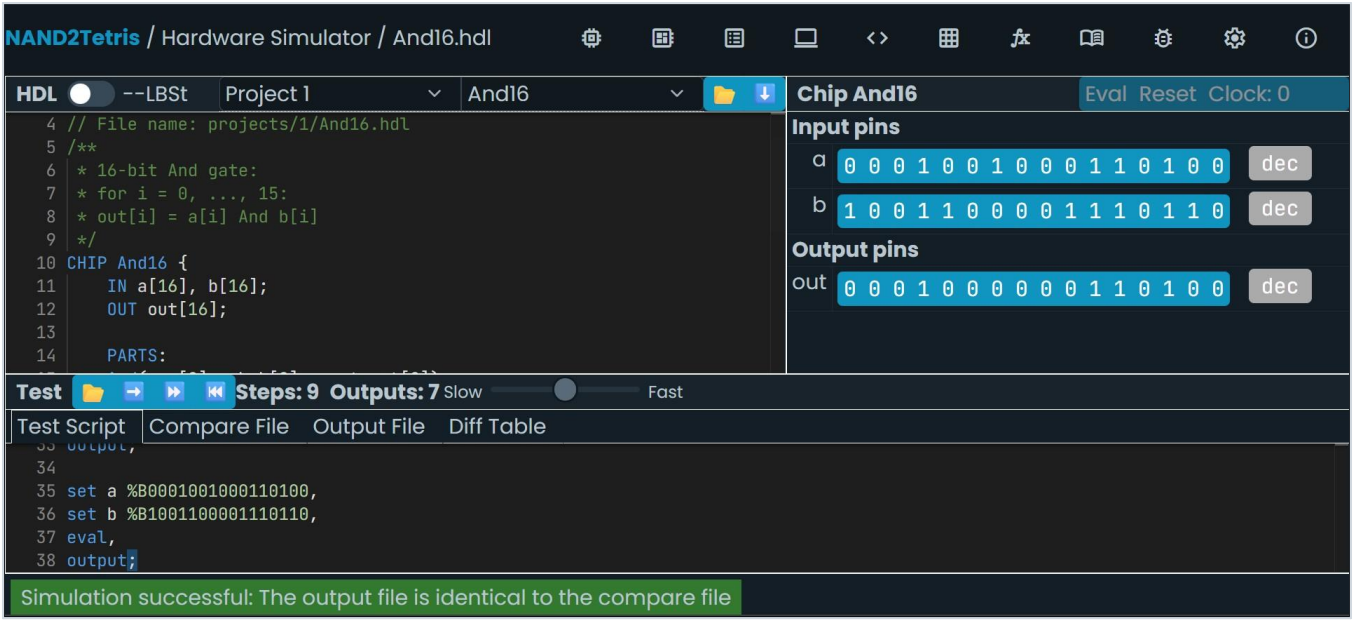

09 Or16.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Or16.hdl
/**
 * 16-bit Or gate:
 * for i = 0, ..., 15:
 * out[i] = a[i] Or b[i]
 */
CHIP Or16 {
    IN a[16], b[16];
    OUT out[16];

    PARTS:
    Or(a=a[0], b=b[0], out=out[0]);
    Or(a=a[1], b=b[1], out=out[1]);
    Or(a=a[2], b=b[2], out=out[2]);
    Or(a=a[3], b=b[3], out=out[3]);
    Or(a=a[4], b=b[4], out=out[4]);
    Or(a=a[5], b=b[5], out=out[5]);
    Or(a=a[6], b=b[6], out=out[6]);
    Or(a=a[7], b=b[7], out=out[7]);
    Or(a=a[8], b=b[8], out=out[8]);
    Or(a=a[9], b=b[9], out=out[9]);
    Or(a=a[10], b=b[10], out=out[10]);
    Or(a=a[11], b=b[11], out=out[11]);
    Or(a=a[12], b=b[12], out=out[12]);
    Or(a=a[13], b=b[13], out=out[13]);
    Or(a=a[14], b=b[14], out=out[14]);
    Or(a=a[15], b=b[15], out=out[15]);
}
```

Screenshot (Hardware Simulator output):

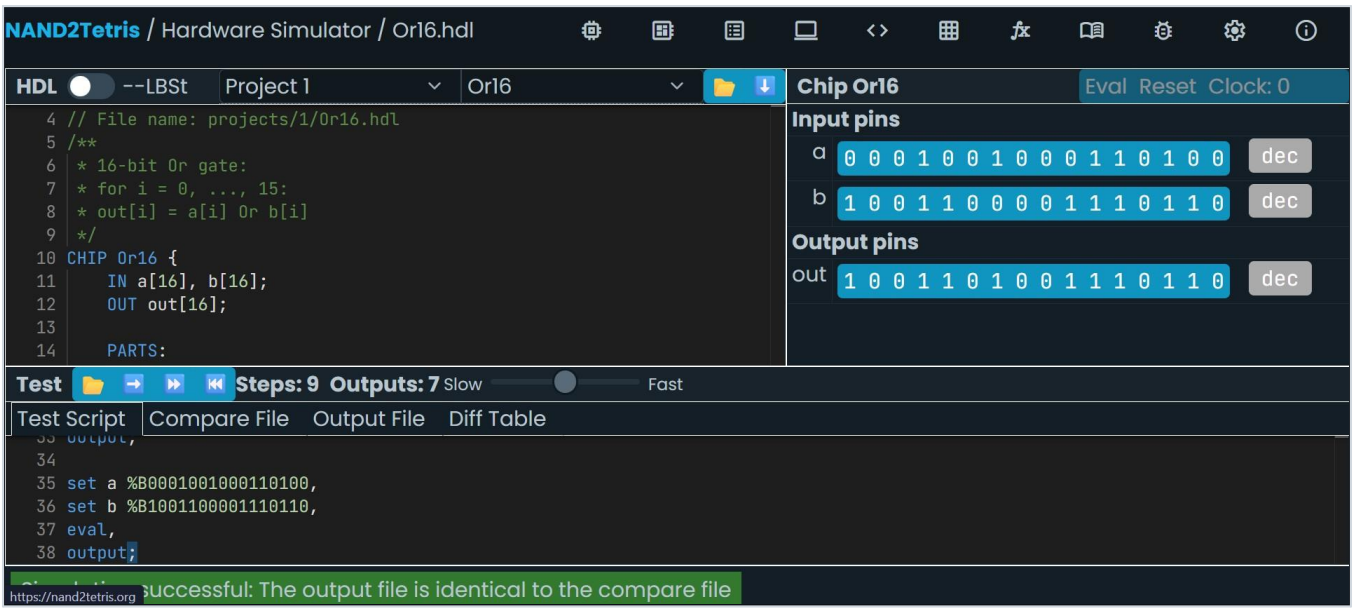

10 Mux16.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Mux16.hdl
/**
 * 16-bit multiplexor:
 * for i = 0, ..., 15:
 * if (sel = 0) out[i] = a[i], else out[i] = b[i]
 */
CHIP Mux16 {
    IN a[16], b[16], sel;
    OUT out[16];

    PARTS:
    Mux(a=a[0], b=b[0], sel=sel, out=out[0]);
    Mux(a=a[1], b=b[1], sel=sel, out=out[1]);
    Mux(a=a[2], b=b[2], sel=sel, out=out[2]);
    Mux(a=a[3], b=b[3], sel=sel, out=out[3]);
    Mux(a=a[4], b=b[4], sel=sel, out=out[4]);
    Mux(a=a[5], b=b[5], sel=sel, out=out[5]);
    Mux(a=a[6], b=b[6], sel=sel, out=out[6]);
    Mux(a=a[7], b=b[7], sel=sel, out=out[7]);
    Mux(a=a[8], b=b[8], sel=sel, out=out[8]);
    Mux(a=a[9], b=b[9], sel=sel, out=out[9]);
    Mux(a=a[10], b=b[10], sel=sel, out=out[10]);
    Mux(a=a[11], b=b[11], sel=sel, out=out[11]);
    Mux(a=a[12], b=b[12], sel=sel, out=out[12]);
    Mux(a=a[13], b=b[13], sel=sel, out=out[13]);
    Mux(a=a[14], b=b[14], sel=sel, out=out[14]);
    Mux(a=a[15], b=b[15], sel=sel, out=out[15]);
}
```

Screenshot (Hardware Simulator output):

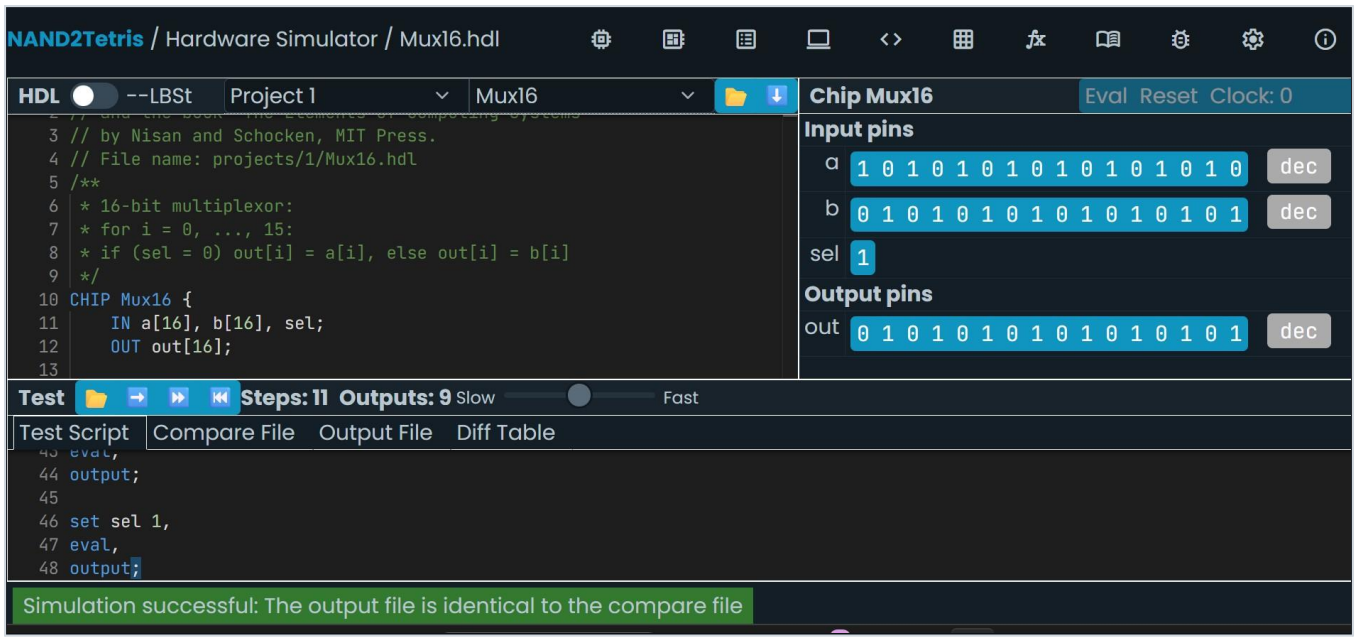

11 Or8Way.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Or8Way.hdl
/**
 * 8-way Or gate:
 * out = in[0] Or in[1] Or ... Or in[7]
 */
CHIP Or8Way {
    IN in[8];
    OUT out;

    PARTS:
    Or(a=in[0], b=in[1], out=w1);
    Or(a=w1, b=in[2], out=w2);
    Or(a=w2, b=in[3], out=w3);
    Or(a=w3, b=in[4], out=w4);
    Or(a=w4, b=in[5], out=w5);
    Or(a=w5, b=in[6], out=w6);
    Or(a=w6, b=in[7], out=out);
}
```

Screenshot (Hardware Simulator output):

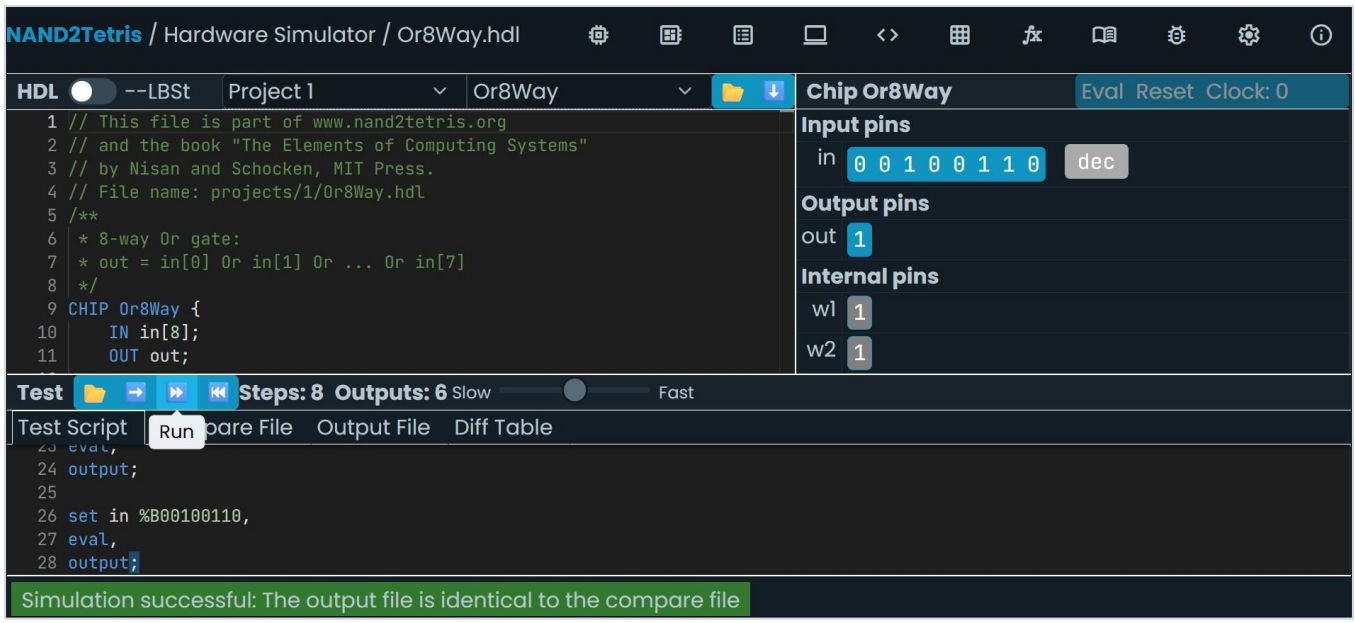

12 Mux4Way16.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Mux4Way16.hdl
/**
 * 4-way 16-bit multiplexor:
 * out = a if sel = 00
 *       b if sel = 01
 *       c if sel = 10
 *       d if sel = 11
 */
CHIP Mux4Way16 {
    IN a[16], b[16], c[16], d[16], sel[2];
    OUT out[16];

    PARTS:
    Mux16(a=a, b=b, sel=sel[0], out=muxAB);
    Mux16(a=c, b=d, sel=sel[0], out=muxCD);
    Mux16(a=muxAB, b=muxCD, sel=sel[1], out=out);
}
```

Screenshot (Hardware Simulator output):

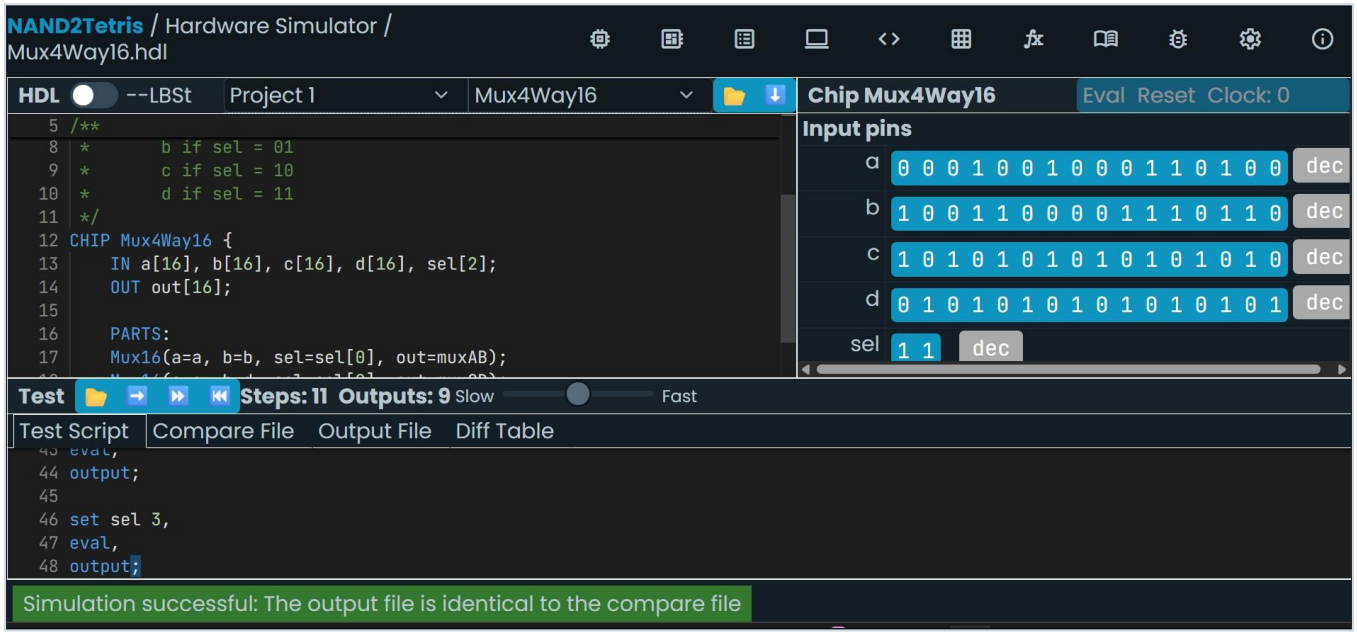

13 Mux8Way16.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/Mux8Way16.hdl
/**
 * 8-way 16-bit multiplexor:
 * out = a if sel = 000
 *       b if sel = 001
 *       c if sel = 010
 *       d if sel = 011
 *       e if sel = 100
 *       f if sel = 101
 *       g if sel = 110
 *       h if sel = 111
 */
CHIP Mux8Way16 {
    IN a[16], b[16], c[16], d[16],
       e[16], f[16], g[16], h[16],
       sel[3];
    OUT out[16];

    PARTS:
    Mux4Way16(a=a, b=b, c=c, d=d, sel=sel[0..1], out=outABCD);
    Mux4Way16(a=e, b=f, c=g, d=h, sel=sel[0..1], out=outEFGH);
    Mux16(a=outABCD, b=outEFGH, sel=sel[2], out=out);
}
```

Screenshot (Hardware Simulator output):

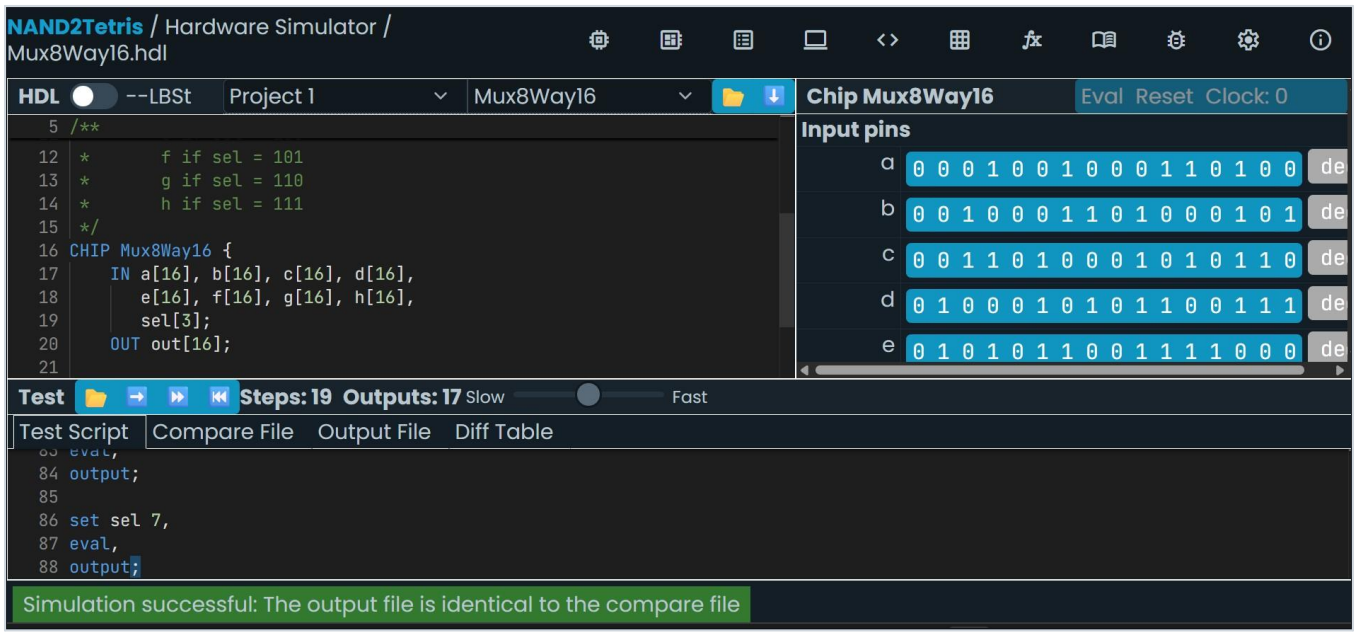

14 DMux4Way.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/DMux4Way.hdl
/**
 * 4-way demultiplexor:
 * [a, b, c, d] = [in, 0, 0, 0] if sel = 00
 *                [0, in, 0, 0] if sel = 01
 *                [0, 0, in, 0] if sel = 10
 *                [0, 0, 0, in] if sel = 11
 */
CHIP DMux4Way {
    IN in, sel[2];
    OUT a, b, c, d;

    PARTS:
    DMux(in=in, sel=sel[1], a=top, b=bottom);
    DMux(in=top, sel=sel[0], a=a, b=b);
    DMux(in=bottom, sel=sel[0], a=c, b=d);
}
```

Screenshot (Hardware Simulator output):

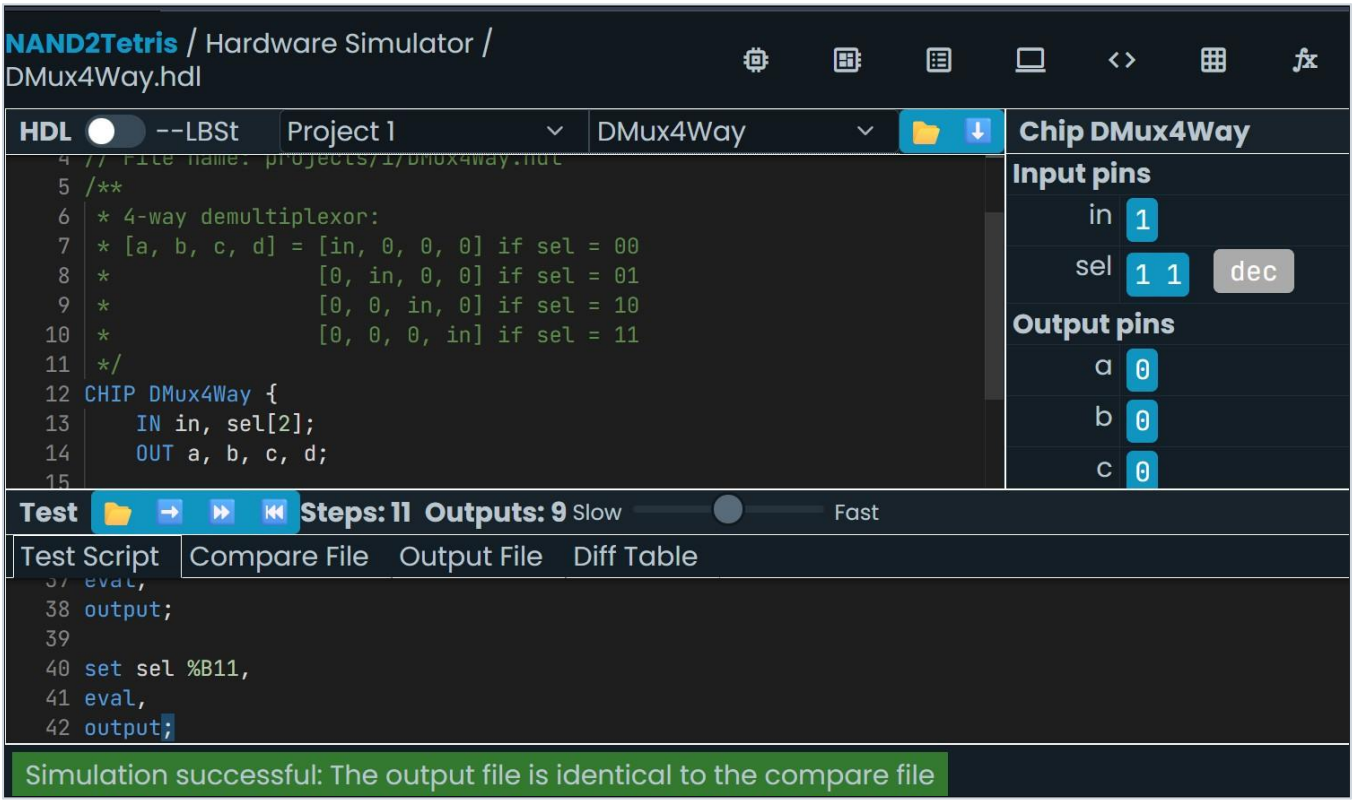

15 DMux8Way.hdl


PROJECT 1

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/1/DMux8Way.hdl
/**
 * 8-way demultiplexor:
 * [a, b, c, d, e, f, g, h] = [in, 0,  0,  0,  0,  0,  0,  0] if sel = 000
 *                            [0, in,  0,  0,  0,  0,  0,  0] if sel = 001
 *                            [0,  0, in,  0,  0,  0,  0,  0] if sel = 010
 *                            [0,  0,  0, in,  0,  0,  0,  0] if sel = 011
 *                            [0,  0,  0,  0, in,  0,  0,  0] if sel = 100
 *                            [0,  0,  0,  0,  0, in,  0,  0] if sel = 101
 *                            [0,  0,  0,  0,  0,  0, in,  0] if sel = 110
 *                            [0,  0,  0,  0,  0,  0,  0, in] if sel = 111
 */
CHIP DMux8Way {
    IN in, sel[3];
    OUT a, b, c, d, e, f, g, h;

    PARTS:
    DMux(in=in, sel=sel[2], a=topGroup, b=bottomGroup);
    DMux4Way(in=topGroup, sel=sel[0..1], a=a, b=b, c=c, d=d);
    DMux4Way(in=bottomGroup, sel=sel[0..1], a=e, b=f, c=g, d=h);
}
```

Screenshot (Hardware Simulator output):

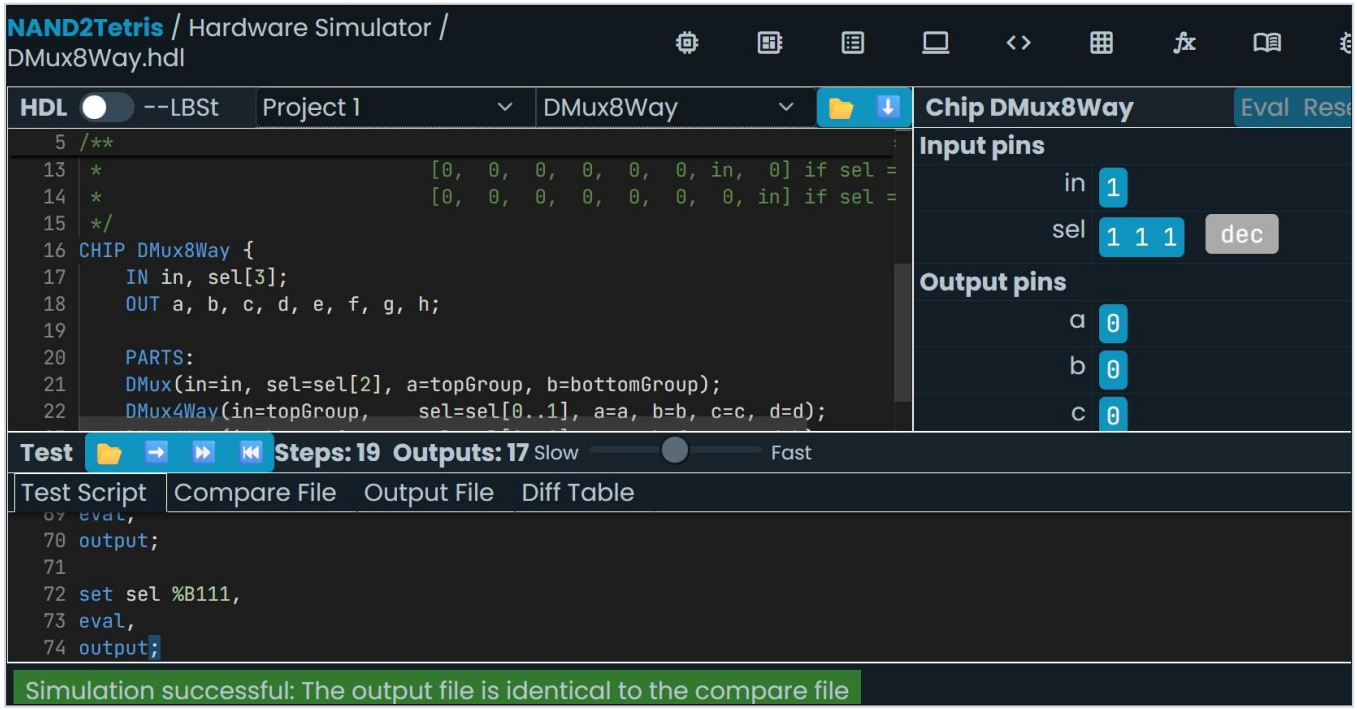

16 HalfAdder.hdl


PROJECT 2

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/2/HalfAdder.hdl
/**
 * Computes the sum of two bits.
 */
CHIP HalfAdder {
    IN a, b;    // 1-bit inputs
    OUT sum,    // Right bit of a + b
        carry;  // Left bit of a + b

    PARTS:
    Xor(a=a, b=b, out=sum);
    And(a=a, b=b, out=carry);
}
```

Screenshot (Hardware Simulator output):

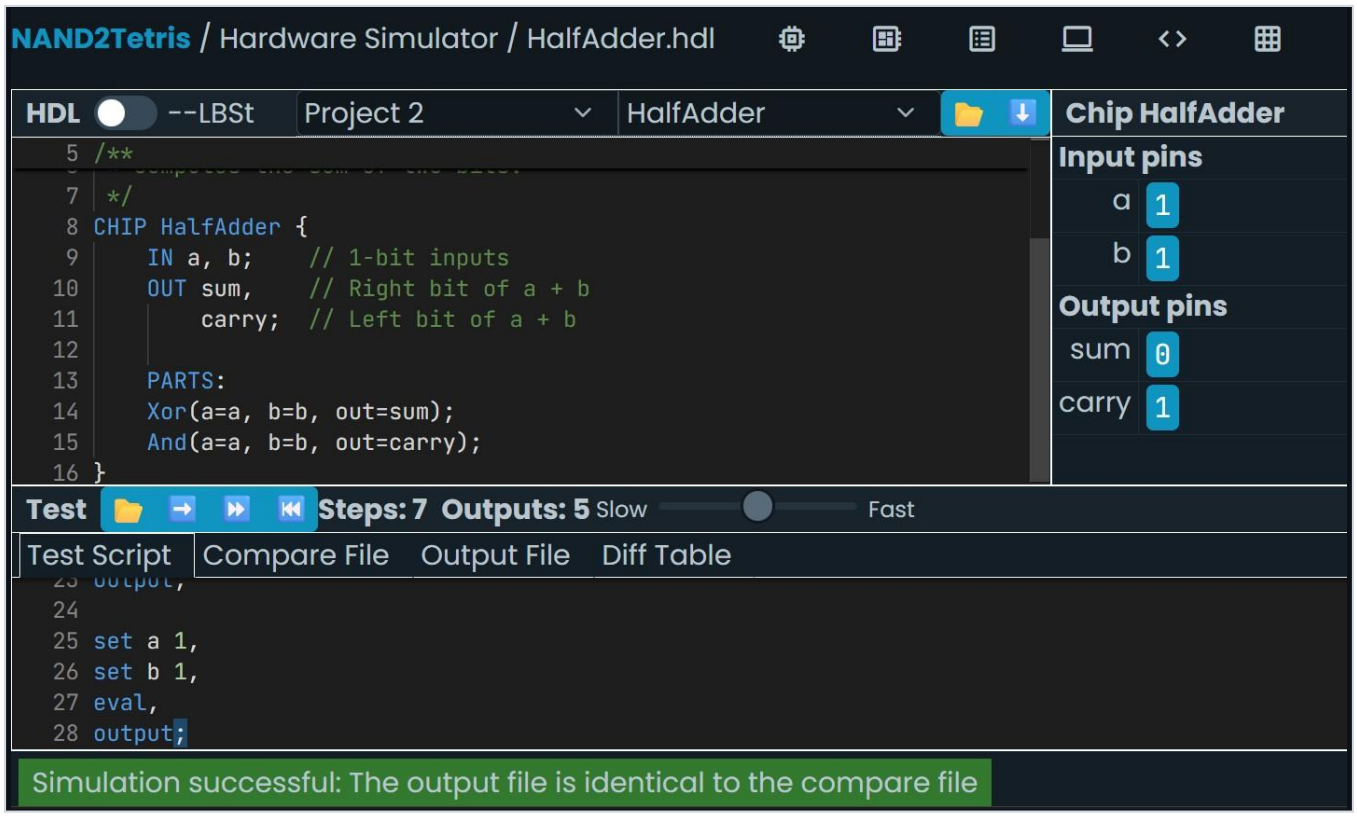

17 FullAdder.hdl


PROJECT 2

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/2/FullAdder.hdl
/**
 * Computes the sum of three bits.
 */
CHIP FullAdder {
    IN a, b, c;  // 1-bit inputs
    OUT sum,     // Right bit of a + b + c
        carry;   // Left bit of a + b + c

    PARTS:
    HalfAdder(a=a, b=b, sum=s1, carry=c1);
    HalfAdder(a=s1, b=c, sum=sum, carry=c2);
    Or(a=c1, b=c2, out=carry);
}
```

Screenshot (Hardware Simulator output):

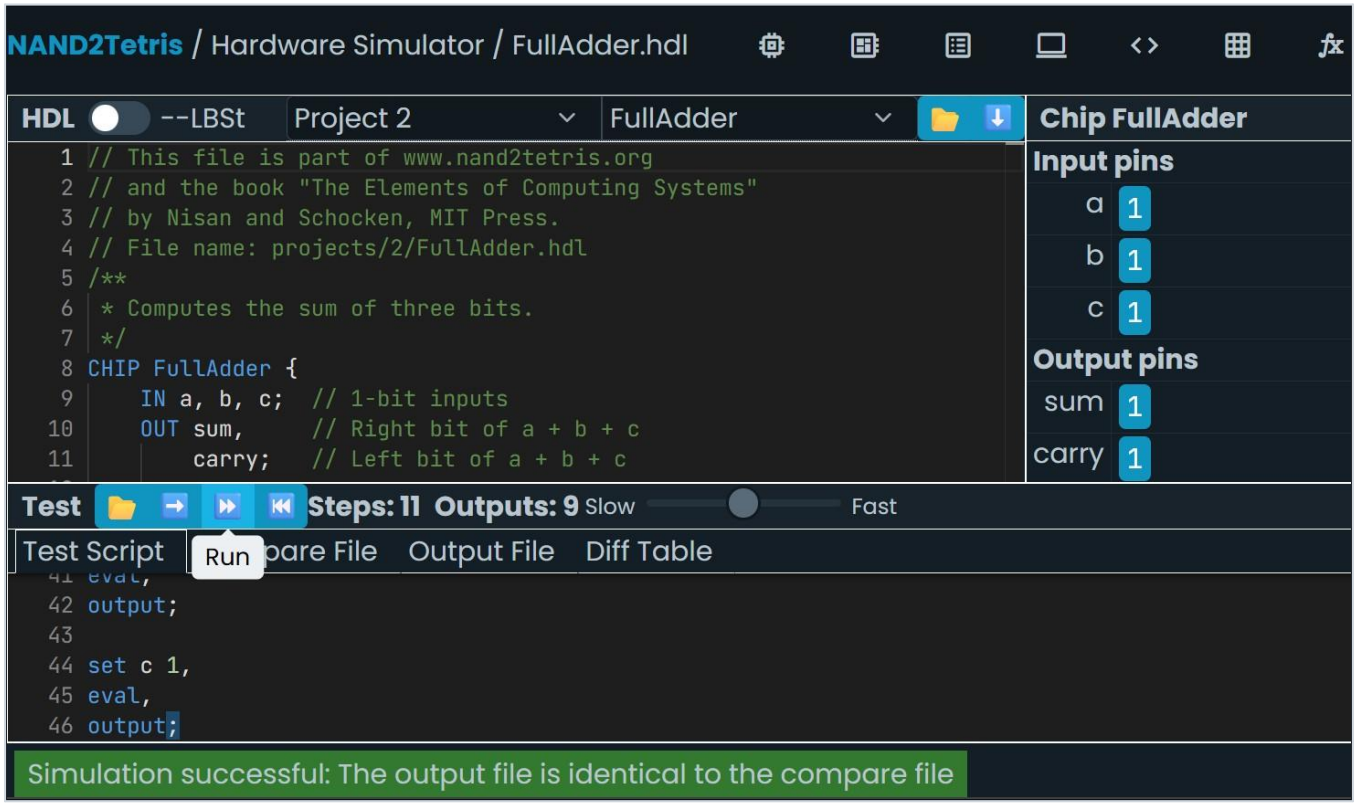

18 Add16.hdl


PROJECT 2

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/2/Add16.hdl
/**
 * 16-bit adder: Adds two 16-bit two's complement values.
 * The most significant carry bit is ignored.
 */
CHIP Add16 {
    IN a[16], b[16];
    OUT out[16];

    PARTS:
    HalfAdder(a=a[0], b=b[0], sum=out[0], carry=c0);
    FullAdder(a=a[1], b=b[1], c=c0, sum=out[1], carry=c1);
    FullAdder(a=a[2], b=b[2], c=c1, sum=out[2], carry=c2);
    FullAdder(a=a[3], b=b[3], c=c2, sum=out[3], carry=c3);
    FullAdder(a=a[4], b=b[4], c=c3, sum=out[4], carry=c4);
    FullAdder(a=a[5], b=b[5], c=c4, sum=out[5], carry=c5);
    FullAdder(a=a[6], b=b[6], c=c5, sum=out[6], carry=c6);
    FullAdder(a=a[7], b=b[7], c=c6, sum=out[7], carry=c7);
    FullAdder(a=a[8], b=b[8], c=c7, sum=out[8], carry=c8);
    FullAdder(a=a[9], b=b[9], c=c8, sum=out[9], carry=c9);
    FullAdder(a=a[10], b=b[10], c=c9, sum=out[10], carry=c10);
    FullAdder(a=a[11], b=b[11], c=c10, sum=out[11], carry=c11);
    FullAdder(a=a[12], b=b[12], c=c11, sum=out[12], carry=c12);
    FullAdder(a=a[13], b=b[13], c=c12, sum=out[13], carry=c13);
    FullAdder(a=a[14], b=b[14], c=c13, sum=out[14], carry=c14);
    FullAdder(a=a[15], b=b[15], c=c14, sum=out[15], carry=c15);
}
```

Screenshot (Hardware Simulator output):

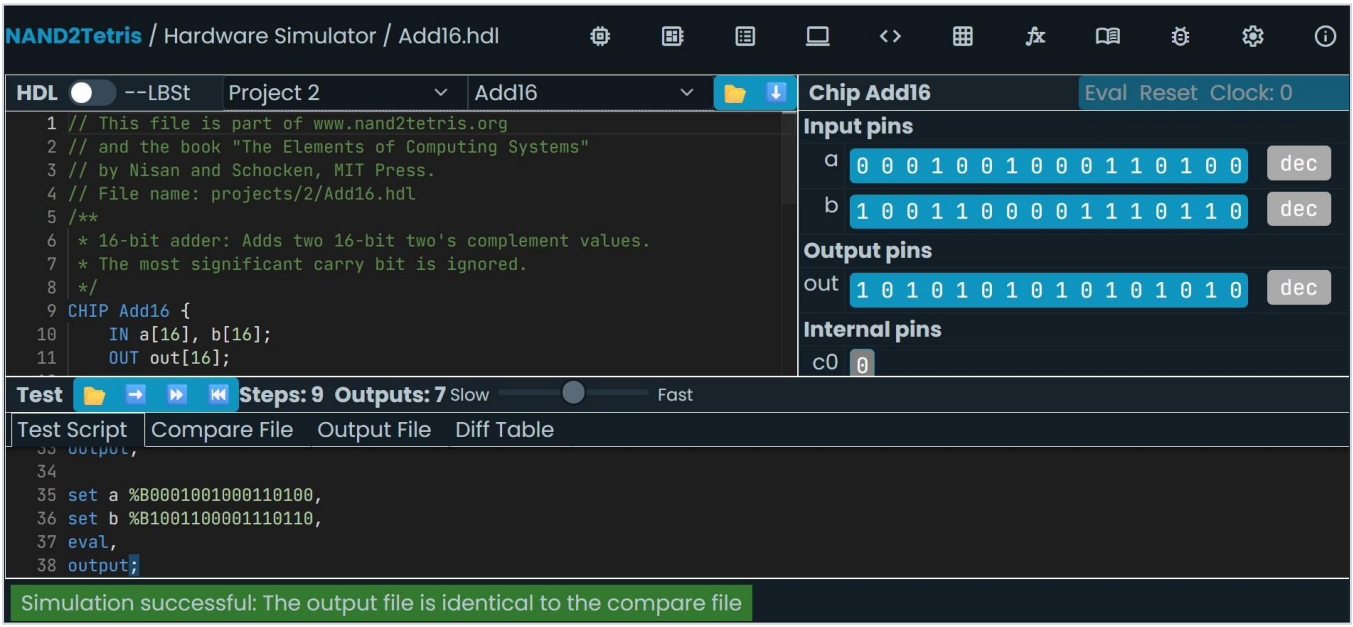

19 Inc16.hdl


PROJECT 2

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/2/Inc16.hdl
/**
 * 16-bit incrementer:
 * out = in + 1
 */
CHIP Inc16 {
    IN in[16];
    OUT out[16];

    PARTS:
    Add16(a=in, b[0]=true, out=out);
}
```

Screenshot (Hardware Simulator output):

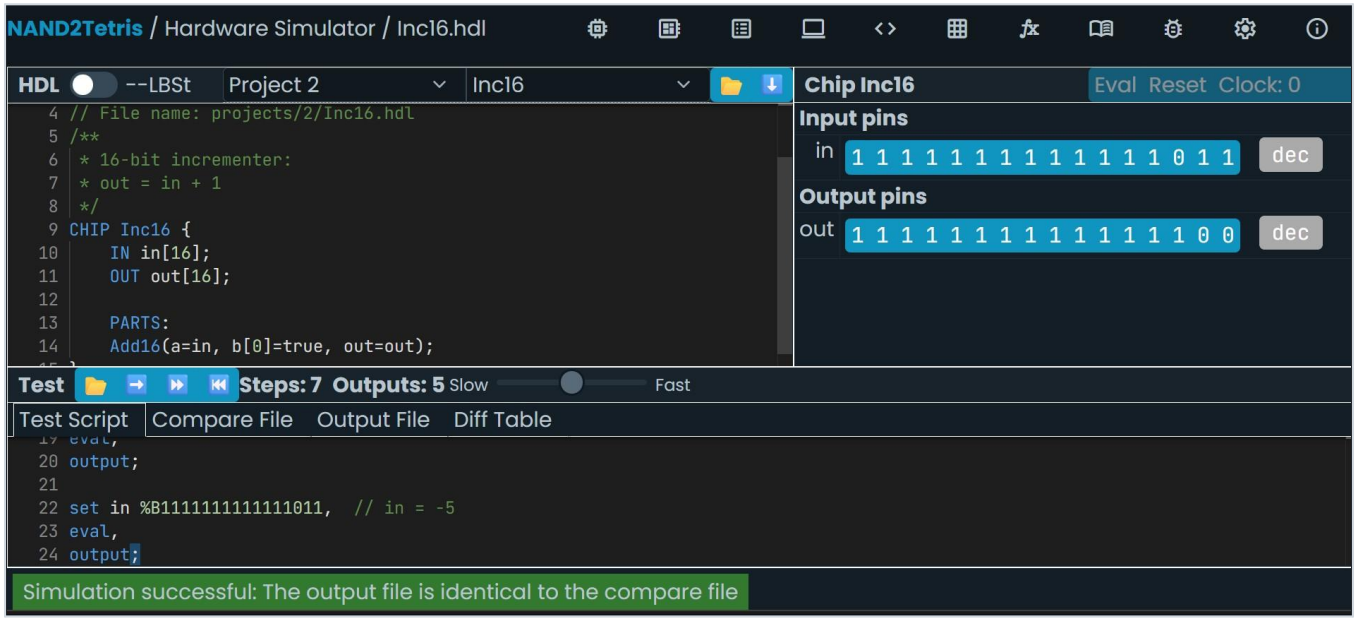

Code:

```
// This file is part of www.nand2tetris.org
// and the book "The Elements of Computing Systems"
// by Nisan and Schocken, MIT Press.
// File name: projects/2/ALU.hdl
/**
 * ALU (Arithmetic Logic Unit):
 * Computes out = one of the following functions:
 *                0, 1, -1,
 *                x, y, !x, !y, -x, -y,
 *                x + 1, y + 1, x - 1, y - 1,
 *                x + y, x - y, y - x,
 *                x & y, x | y
 * on the 16-bit inputs x, y,
 * according to the input bits zx, nx, zy, ny, f, no.
 * In addition, computes the two output bits:
 * if (out == 0) zr = 1, else zr = 0
 * if (out < 0)  ng = 1, else ng = 0
 */
// Implementation: Manipulates the x and y inputs
// and operates on the resulting values, as follows:
// if (zx == 1) sets x = 0        // 16-bit constant
// if (nx == 1) sets x = !x       // bitwise not
// if (zy == 1) sets y = 0        // 16-bit constant
// if (ny == 1) sets y = !y       // bitwise not
// if (f == 1)  sets out = x + y  // integer 2's complement addition
// if (f == 0)  sets out = x & y  // bitwise and
// if (no == 1) sets out = !out   // bitwise not

CHIP ALU {
    IN
        x[16], y[16],  // 16-bit inputs
        zx, // zero the x input?
        nx, // negate the x input?
        zy, // zero the y input?
        ny, // negate the y input?
        f,  // compute (out = x + y) or (out = x & y)?
        no; // negate the out output?
    OUT
        out[16], // 16-bit output
        zr,      // if (out == 0) equals 1, else 0
        ng;      // if (out < 0)  equals 1, else 0

    PARTS:
    // x zero / negate
    Mux16(a=x, sel=zx, out=x1);
    Not16(in=x1, out=negatedX);
    Mux16(a=x1, b=negatedX, sel=nx, out=x2);

    // y zero / negate
    Mux16(a=y, sel=zy, out=y1);
    Not16(in=y1, out=negatedY);
    Mux16(a=y1, b=negatedY, sel=ny, out=y2);


    // x + y OR x & y
    Add16(a=x2, b=y2, out=added);
    And16(a=x2, b=y2, out=xyAnd);
    Mux16(a=xyAnd, b=added, sel=f, out=result);

    // negate the output?
    Not16(in=result, out=negatedResult);
    Mux16(a=result, b=negatedResult, sel=no, out=out, out[15]=firstOut,
          out[0..7]=finalLeft, out[8..15]=finalRight);

    // output == 0 (zr)
    Or8Way(in=finalLeft, out=zrl);
    Or8Way(in=finalRight, out=zrr);
    Or(a=zrl, b=zrr, out=nzr);
    Not(in=nzr, out=zr);

    // output < 0 (ng)
    And(a=firstOut, b=true, out=ng);
}
```

Screenshot (Hardware Simulator output):

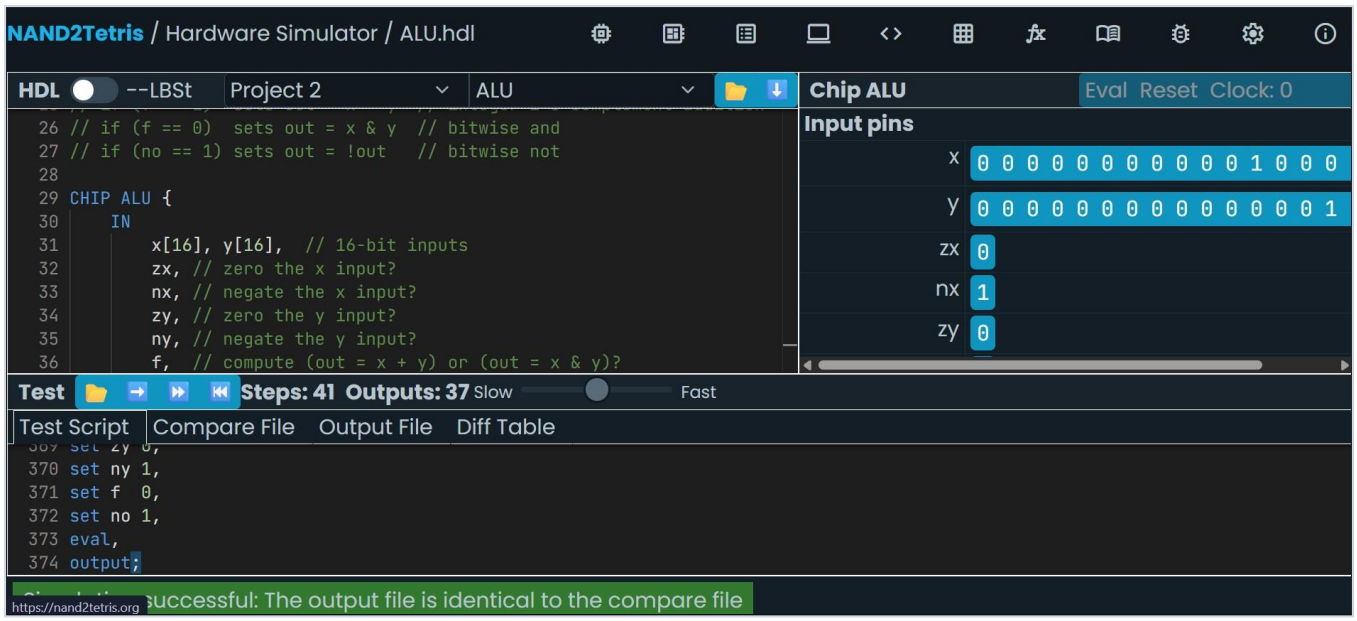

Thank You!