NAND2Tetris - Project 3


Sequential Chips: Hardware Simulator Results

Bit, Register, RAM8, RAM64, RAM512, RAM4K, RAM16K, PC

Name - Prashant kanwal
Roll no - 2501730468

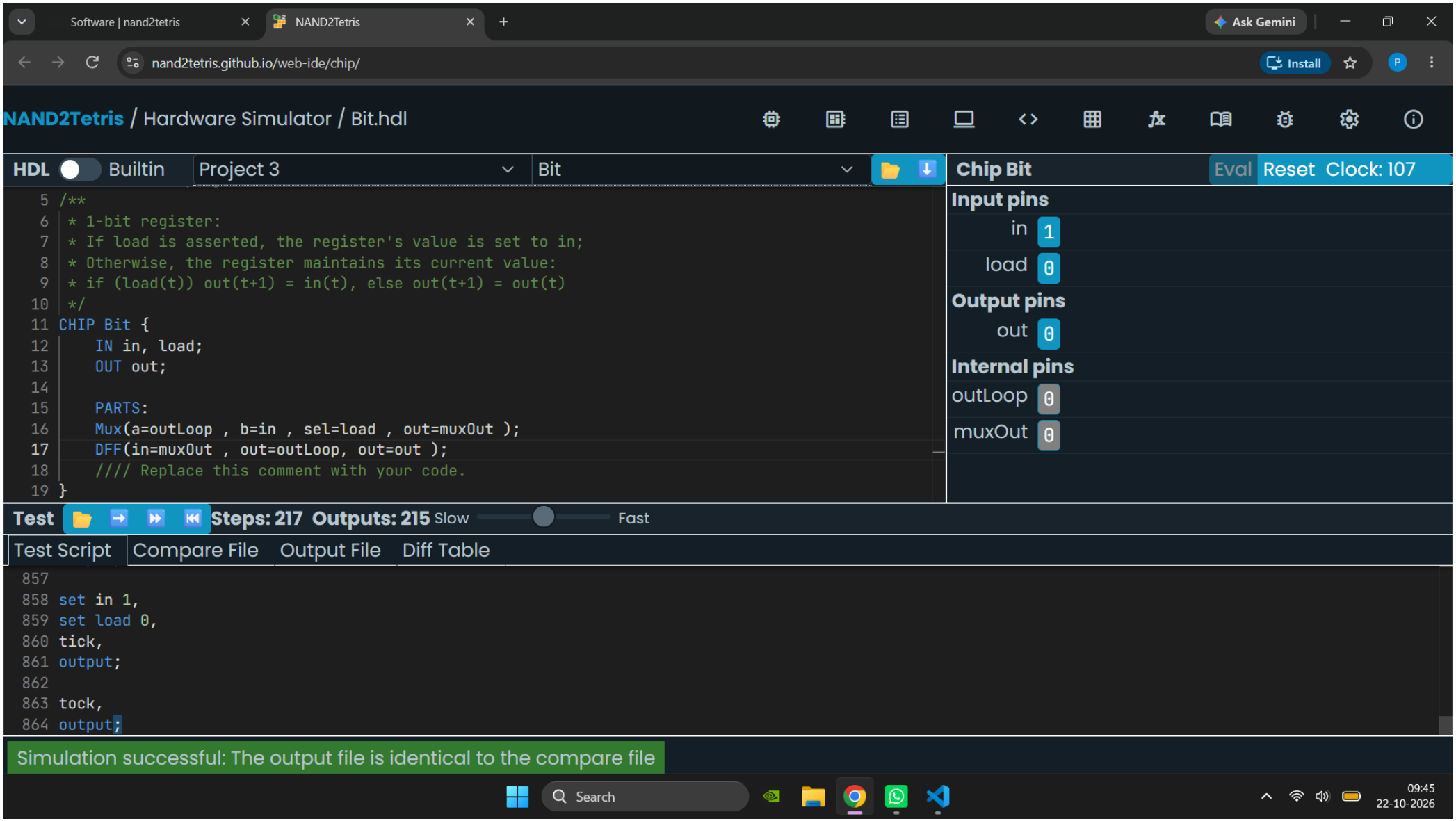
1. Bit.hdl

Simulation successful: output identical to compare file



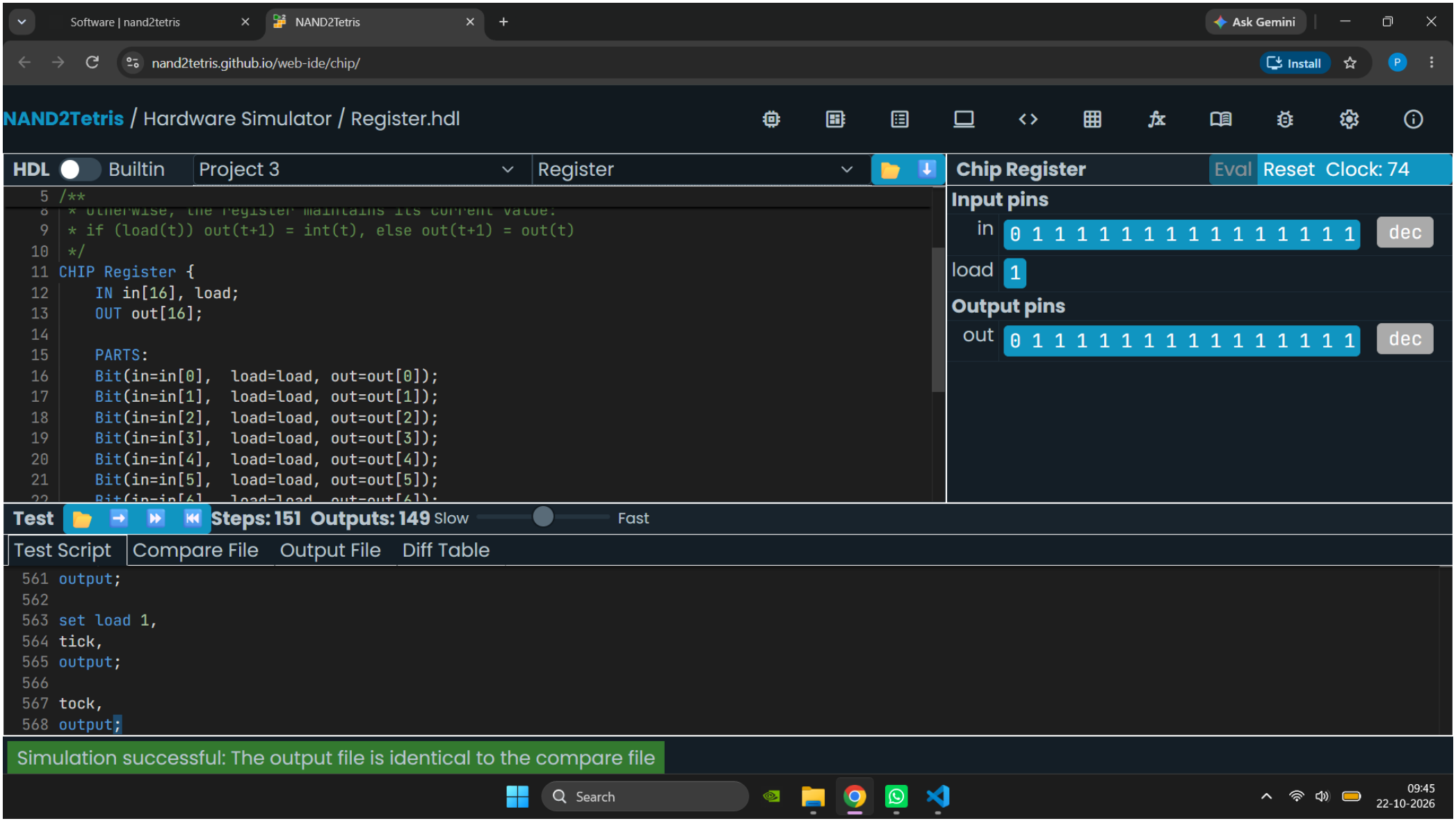
2. Register.hdl

Simulation successful: output identical to compare file



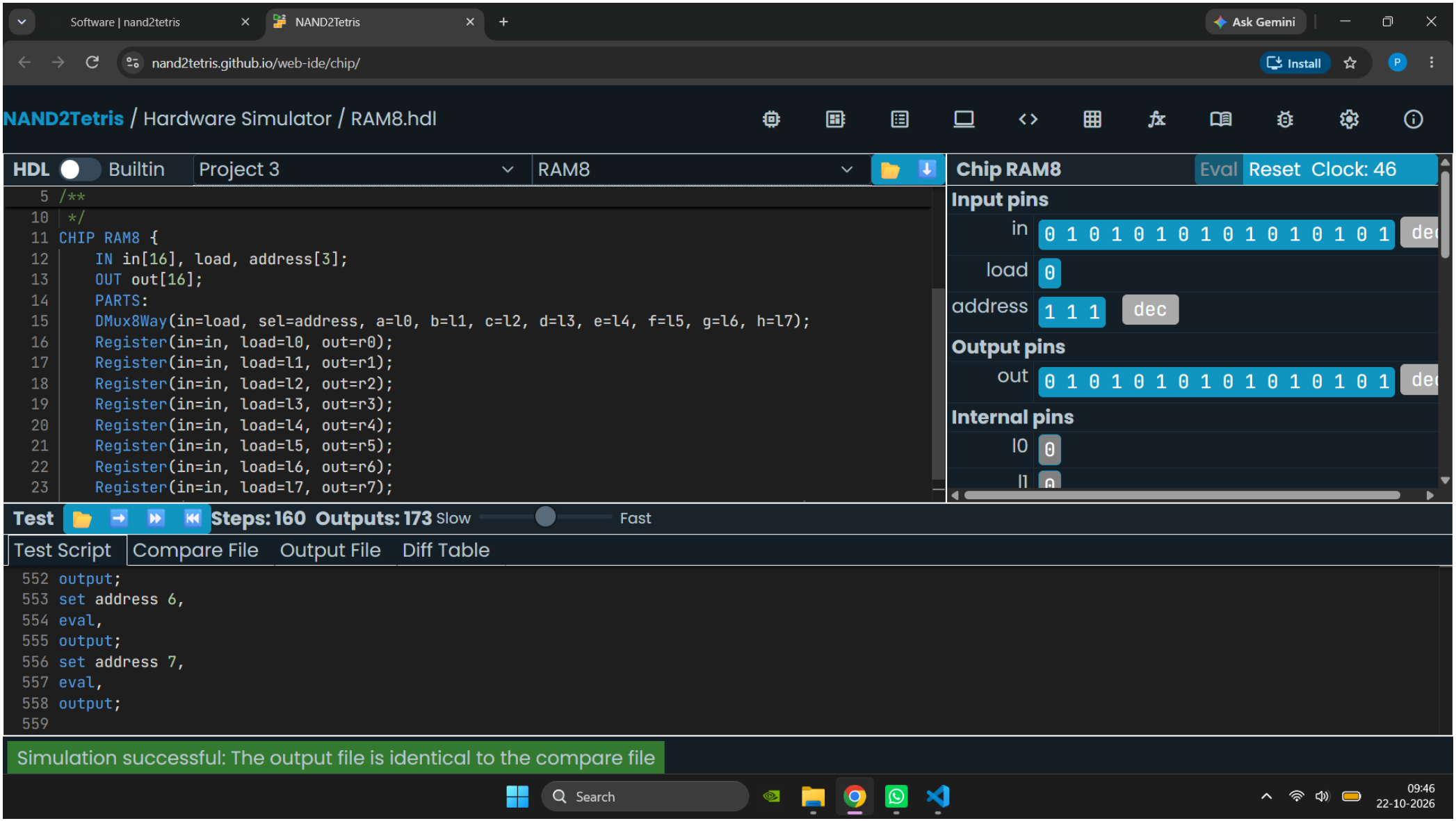
3. RAM8.hdl

Simulation successful: output identical to compare file



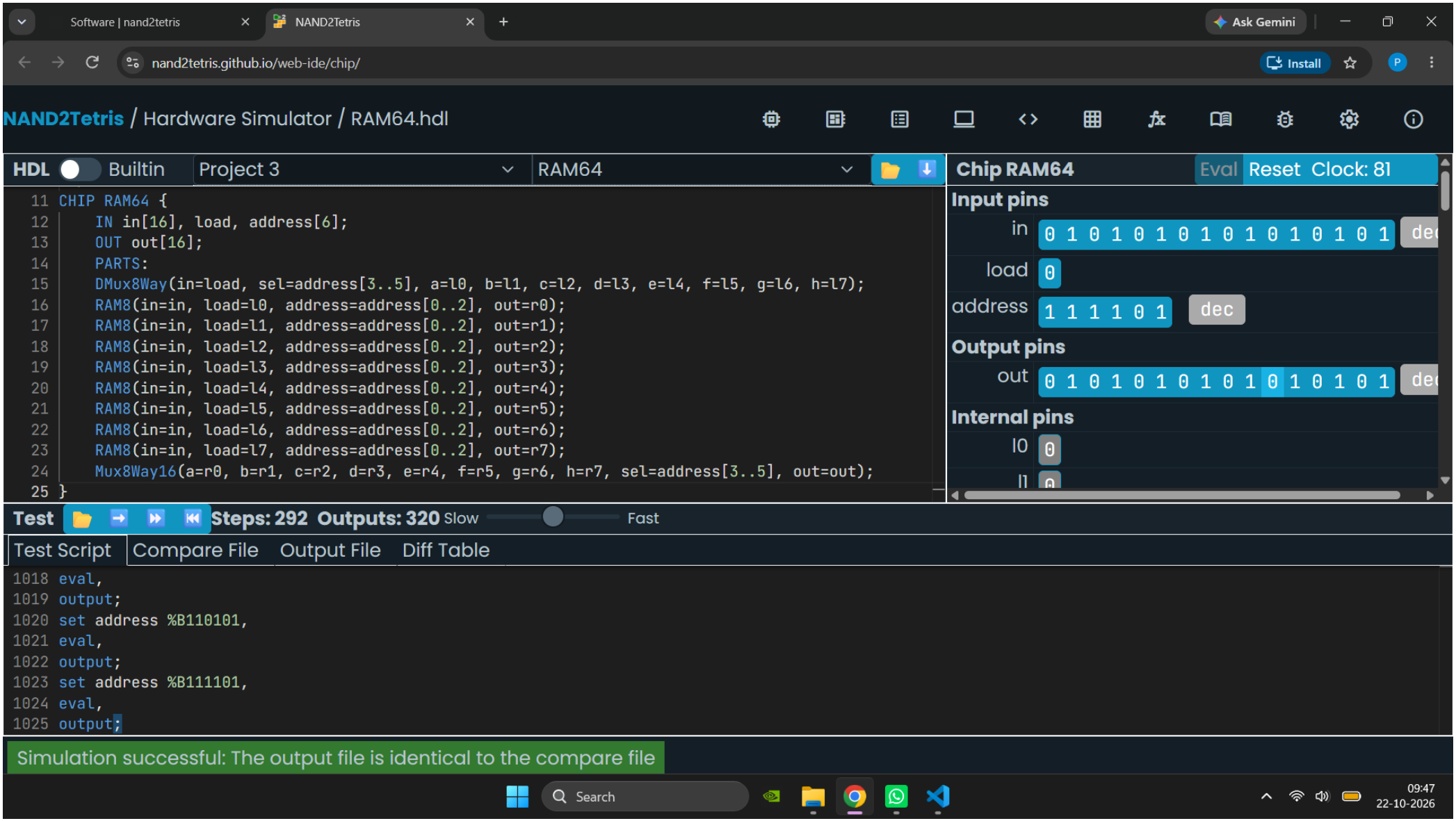
4. RAM64.hdl

Simulation successful: output identical to compare file



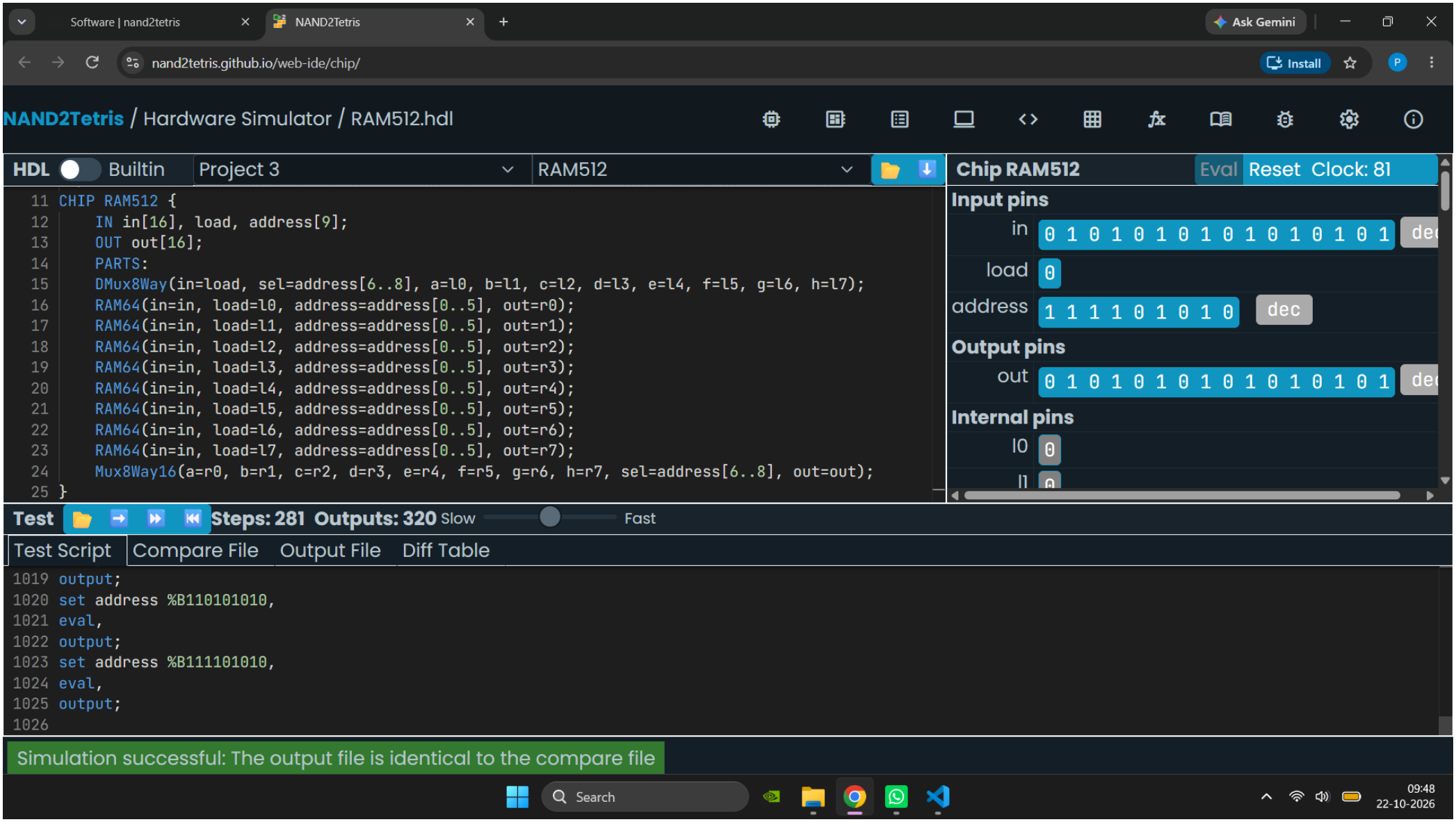
5. RAM512.hdl

Simulation successful: output identical to compare file



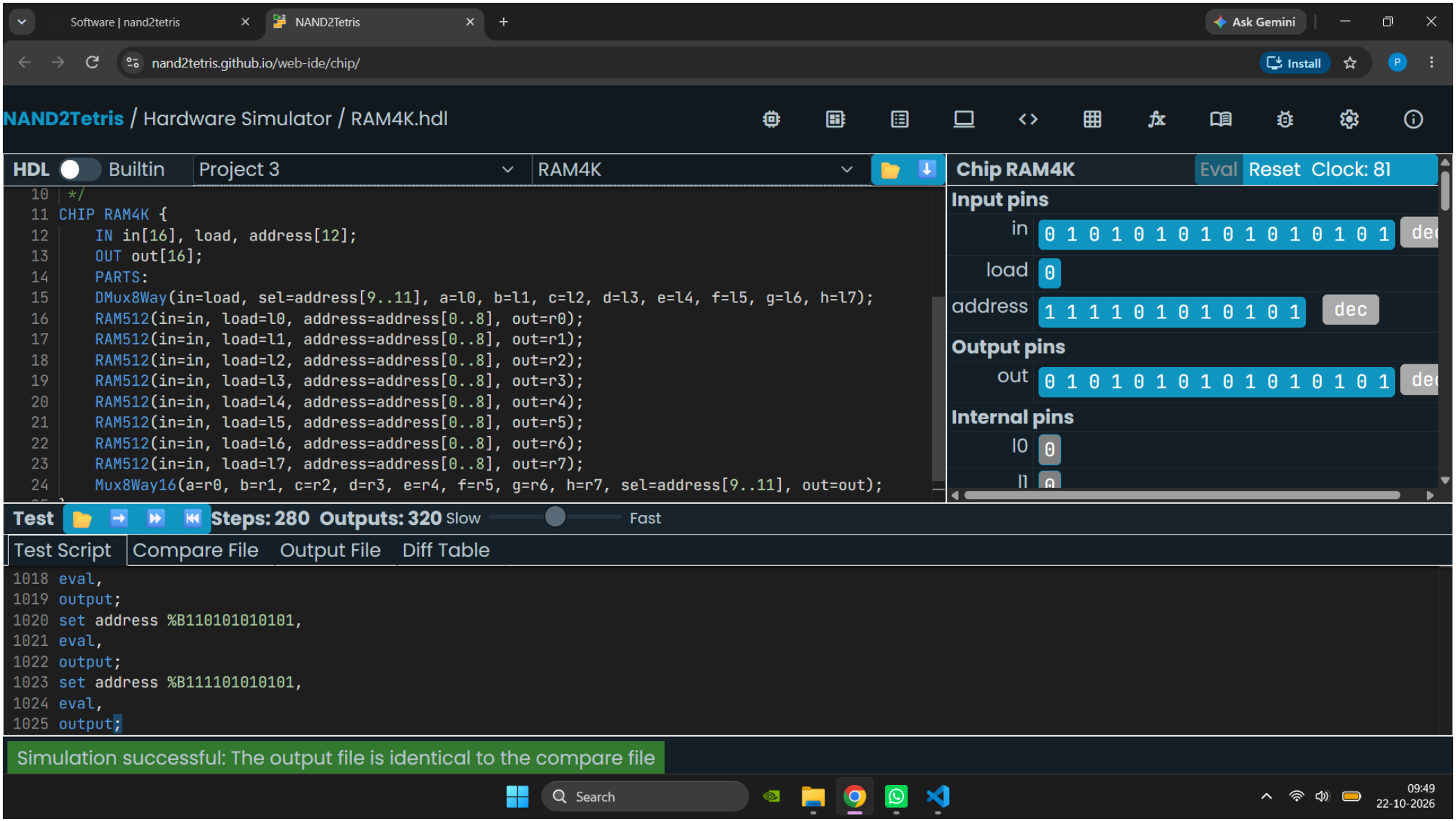
6. RAM4K.hdl

Simulation successful: output identical to compare file



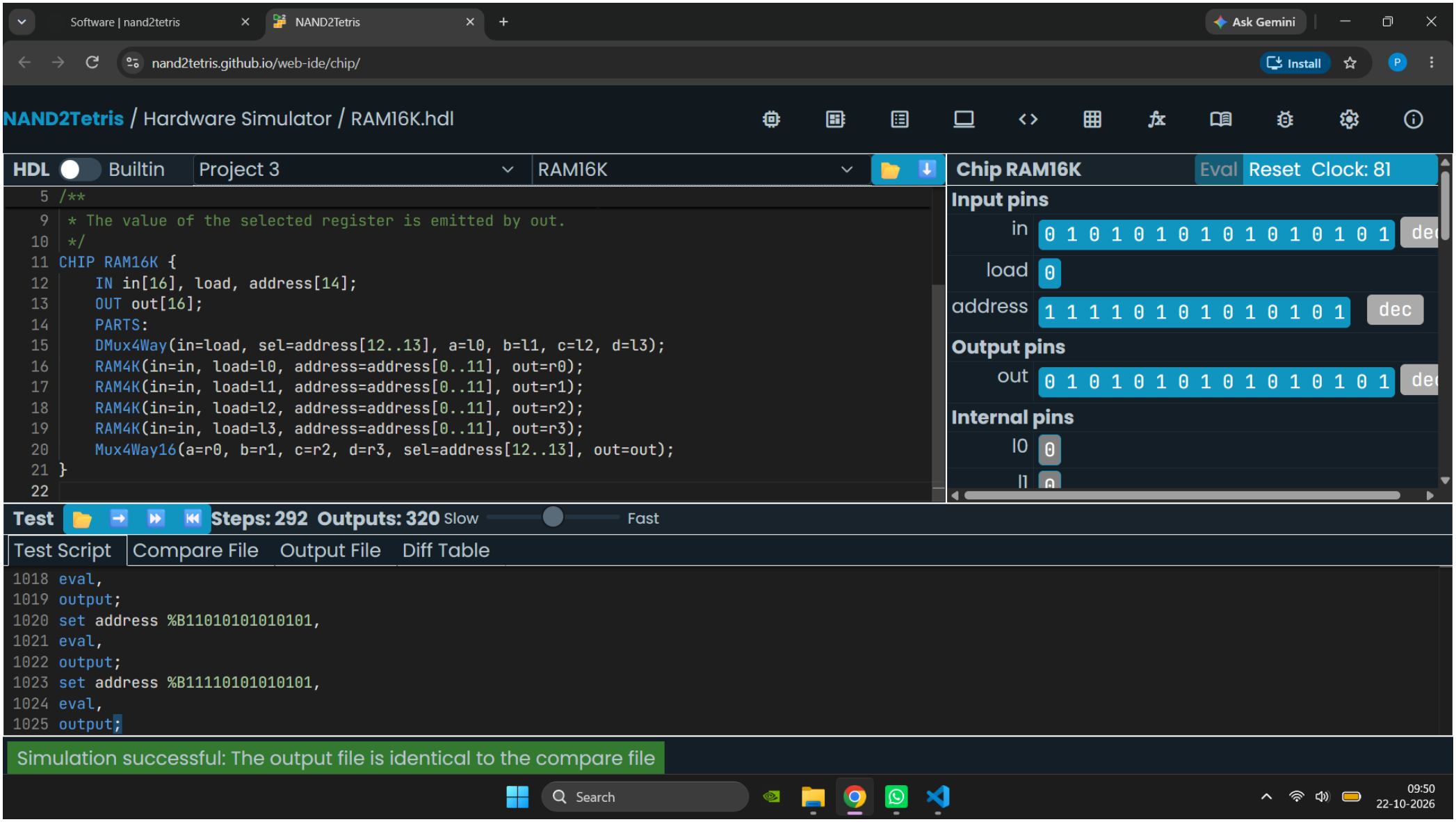7. RAM16K.hdl

Simulation successful: output identical to compare file



8. PC.hdl

Simulation successful: output identical to compare file

